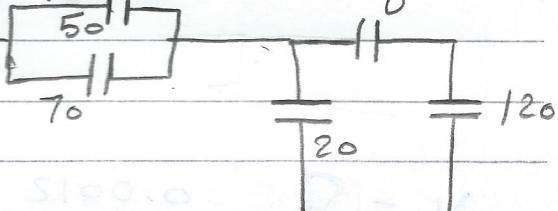



Section 2

$$\frac{6 \times 120}{6+120} = 40 \mu F$$


$$R_{eq} = R_1 + R_2 + R_3$$



$$20 + 40 = 60 \mu F$$

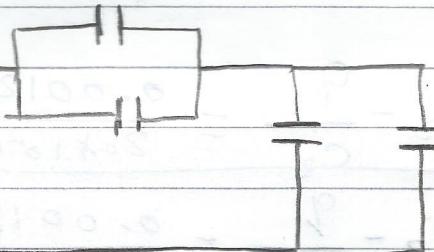
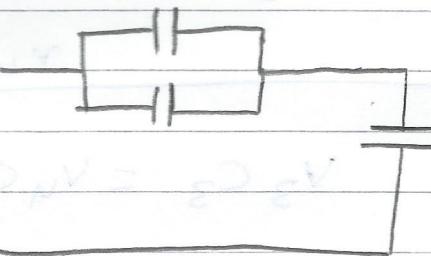
$$C_{eq} = \frac{120 \times 60}{120 + 60} = 40 \mu F$$



$V_s = 120$


$$sV = jV + \bar{V}$$

$$sV = jV + \bar{V}$$

$Dai@du2$

$V_{os} = 120 - 120 \times 0.9 = 12V$

$$C_{eq} = 20 \mu F$$

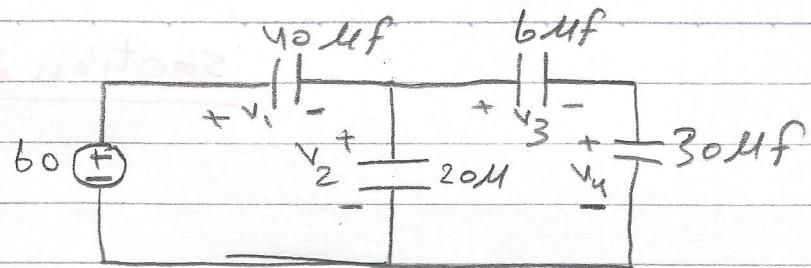

$$\text{total charge } (q) = C_{eq} V$$

$$= 20 \times 10^{-6} \times 60 = 1.2 \text{ mC}$$

$$= 0.0012 \text{ C}$$

$$v_1 = \frac{q}{C_1} = \frac{0.0012}{40 \times 10^{-6}} = 30 \text{ V}$$

$$v_2 = \frac{q}{C_2} = \frac{0.0012}{20 \times 10^{-6}} = 15 \text{ V}$$

$$v_3 = \frac{q}{C_3} = \frac{0.0012}{60 \times 10^{-6}} = 20 \text{ V}$$

$$v_4 = 20$$

$$v_3 C_3 = v_4 C_4$$

$$v_3 \times 60 = v_4 \times 30$$

$$\frac{v_3}{v_4} = \frac{30}{60} = \frac{1}{2}$$

$$v_4 = 2 v_3$$

$$v_3 + v_4 = v_2$$

$$v_3 + v_4 = 30 \rightarrow ①$$

$$v_3 + 2v_3 = 30$$

$$\underline{v_3 = 10} \rightarrow 2$$

Sub ② in ①

$$v_3 + v_4 = 30 \Rightarrow 10 + v_4 = 30 \Rightarrow \underline{v_4 = 20 \text{ V}}$$